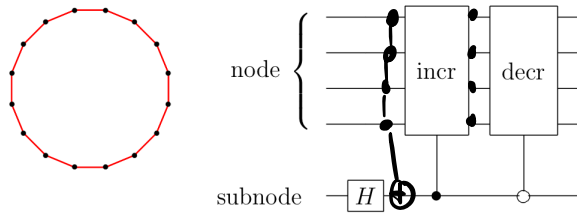


FIG. 1: Increment and decrement gates on  $n$  qubits, producing cyclic permutations in the  $2^n$  bit-string states.



$$0 \quad X \quad L = 2^n - 1$$

$$X = q_0 2^0 + q_1 2^1 + \dots + q_{n-1} 2^{n-1}$$

$$|X\rangle \leftrightarrow |q_0 q_1 \dots q_{n-1}\rangle$$

$$X \mapsto X \pm 1$$

$$(0, 1, 0) = 2 \rightarrow 3 = (1, 1, 0)$$

$$(1, 0, 1) = 5 \rightarrow 4 = (0, 1, 0)$$

$$q \mapsto q^\pm = (q_0^\pm, \dots, q_{n-1}^\pm)$$

$$w/ \quad q_i^+ = \begin{cases} q_i \oplus 1 & \text{if } q_0 = \dots = q_{i-1} = 1 \\ q_i & \text{otherwise} \end{cases}$$

Notation

$\oplus$  is mod 2 addition

$$q_i^- = \begin{cases} q_i \oplus 1 & \text{if } q_0 = \dots = q_{i-1} = 0 \\ q_i & \text{otherwise} \end{cases}$$

Rem

addition by 1 and subtraction by 1 is the same mod 2

Ex ( $n=4$ )

$$X = 11 = 1 \cdot 2^0 + 1 \cdot 2^1 + 0 \cdot 2^2 + 1 \cdot 2^3$$

$$0 \cdot q_0 + \dots + 0 \cdot q_{n-2} + 0 \cdot q_{n-1}$$

$$\rightarrow q = (1, 1, 0, 1)$$

$$\rightarrow q^+ = (0, 0, 1, 1) \quad \& \quad q^- = (0, 1, 0, 1)$$

Eg: ( $n=4$ )

$$x = 8 = 0 \cdot 2^0 + 0 \cdot 2^1 + 0 \cdot 2^2 + 1 \cdot 2^3$$

$$\rightarrow q = (0, 0, 0, 1)$$

$$\rightarrow q^+ = (1, 0, 0, 1) \quad \& \quad q^- = (1, 1, 1, 0)$$

Q: How do we map  $(x, y) \mapsto q = (q_0, \dots, q_{n+m-1})$ ?


$$\bullet \quad 0 \leq x \leq 2^n - 1 \quad \& \quad 0 \leq y \leq 2^m - 1$$

$$\bullet \quad N = 2^n \quad \& \quad M = 2^m$$


$$\bullet \quad (x, y) = (2^0 \cdot q_0 + \dots + 2^{n-1} q_{n-1}, 2^0 p_0 + 2^1 p_1 + \dots + 2^{m-1} p_{m-1})$$

$$\mapsto (q_0, \dots, q_{n-1}, p_0, \dots, p_{m-1})$$


◦ Increment:

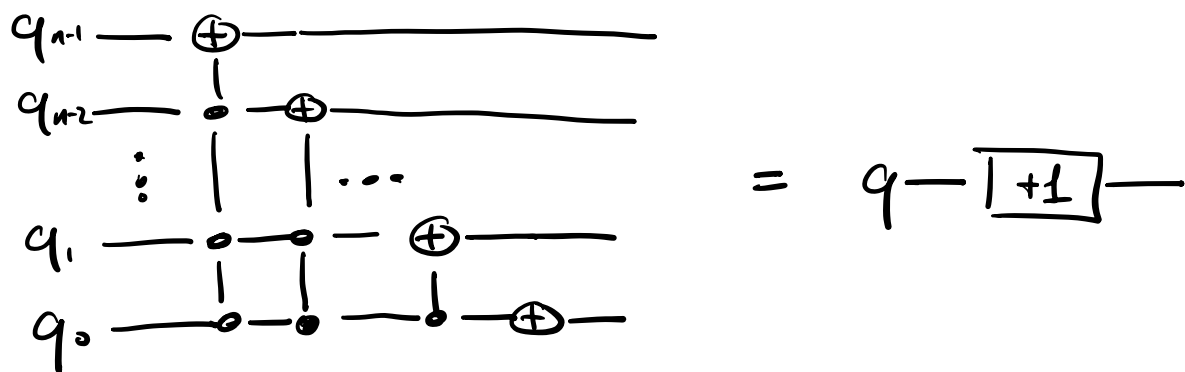


• Decrement:

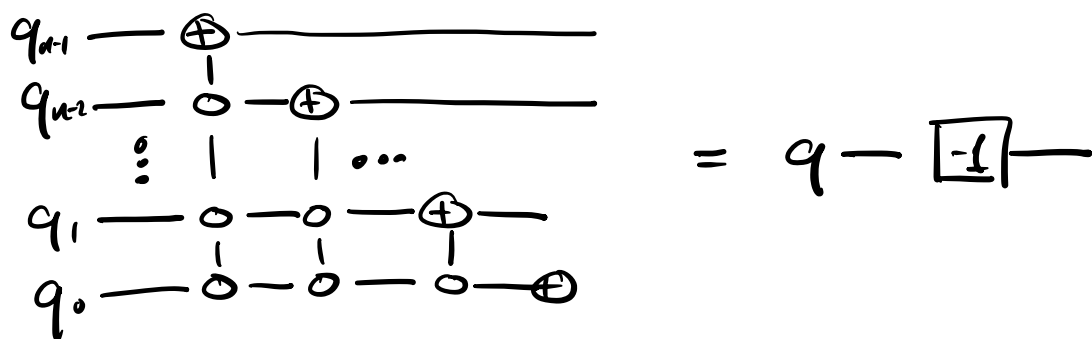


• Control on the last number:

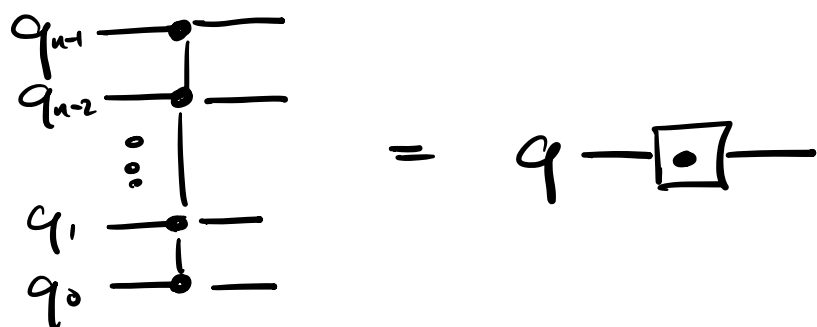

• Control on the first element:

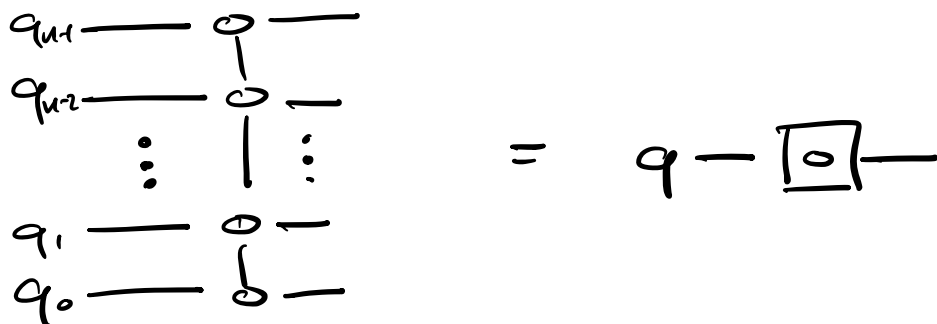

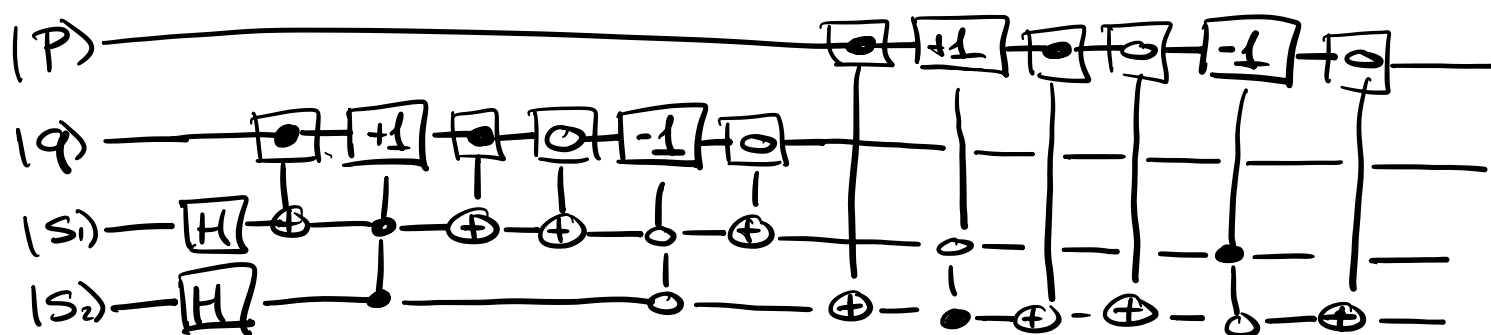- Quantum Circuit for a 2-dimensional (discrete and homogeneous) quantum random walk on a  $2^n \times 2^m$  grid




$$|q\rangle = |q_0, \dots, q_{n-1}\rangle \quad \& \quad |p\rangle = |p_0, \dots, p_{m-1}\rangle$$

$$|S_i\rangle = |S_i\rangle \leftarrow \text{submodule qbits, one qbit each}$$

Req: The controlled gates  $\begin{array}{|c|} \hline \bullet \\ \hline \oplus \end{array}$  &  $\begin{array}{|c|} \hline \circ \\ \hline \oplus \end{array}$  are added to avoid the increments & decrements along the edges,  $N \leftrightarrow 0$  &  $M \leftrightarrow 0$ , respectively.

$$\underline{Eg} \ (N=M=4)$$

$$\begin{aligned} \bullet \ (X, Y) &\mapsto (q_0 2^0 + q_1 2^1 + \dots + q_{n-1} 2^{n-1}, p_0 2^0 + \dots + p_{m-1} 2^{m-1}) \\ &\mapsto |q_0, \dots, q_{n-1}, p_0, \dots, p_{m-1}\rangle \end{aligned}$$

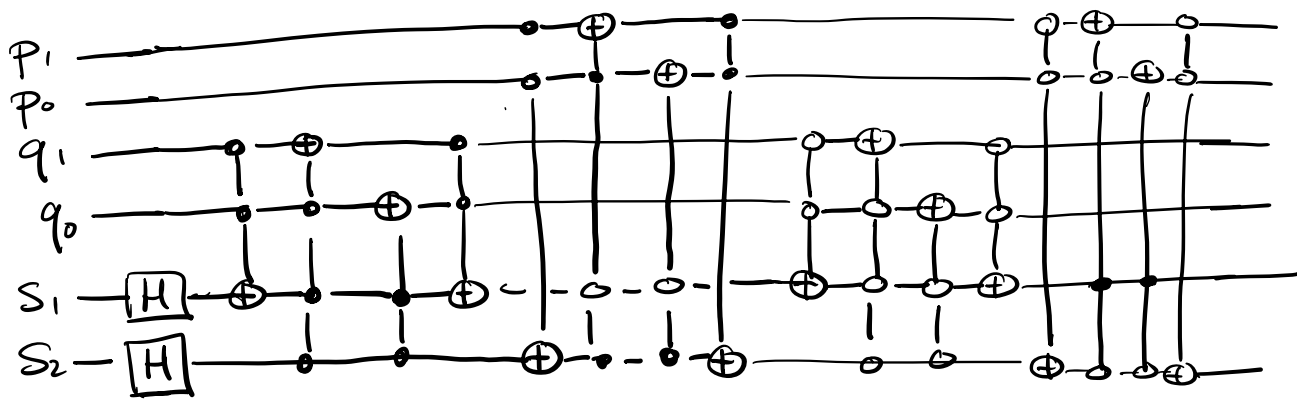

$$|x, y, 0, 0\rangle \xrightarrow{H^{\otimes 2}} \frac{1}{2} (|x, y, 0, 0\rangle + |x, y, 1, 0\rangle + |x, y, 0, 1\rangle + |x, y, 1, 1\rangle)$$

$$(\text{in the bulk}) \mapsto \frac{1}{2} (|x+1, y, 0, 0\rangle + |x, y-1, 1, 0\rangle + |x, y+1, 0, 1\rangle + |x+1, y, 1, 1\rangle)$$